

# PHYSICS LAB MANUAL

2nd Semester



MIDNAPORE CITY COLLEGE

**Course No: C3P: Electricity and Magnetism (Lab)**  
**Credit: 2.**

Sl.No	Experiment	Page No.
1	To study the characteristics of a series RC and RL Circuit.	4
2	To determine an unknown Low Resistance using CROMPTON Potentiometer	11
3	To find low resistance by Carey Fosters bridge	16
4	To determine the resistance of Weston type galvanometer by Kelvin's method using Post Office box.	20
5	Verification of Thevenin's and Norton's Theorems	23
6	Superposition Theorem and Reciprocity Theorem	27
7	Operating Instructions for Anderson's Bridge	34
8	L-C-R Series and Parallel Resonance	39

## **Experiment No. 1**

**Title:** . To study the characteristics of a series RC and RL Circuit.

### **Introduction:**

The RC & RL circuit is used to determine the input and output relationship of voltage and current for different frequencies. In RC series circuit the voltage lags the current by  $90^\circ$  and in RL series circuit the voltage leads the current by  $90^\circ$ .

### **Theory and Methodology:**

#### **RC Series Circuit:**

A resistor-capacitor circuit (RC circuit), or RC network, is an electric circuit composed of resistors and capacitor is in series driven by a voltage or current source (See the figure-1). A first order RC circuit is composed of one resistor and one capacitor and is the simplest type of RC circuit.

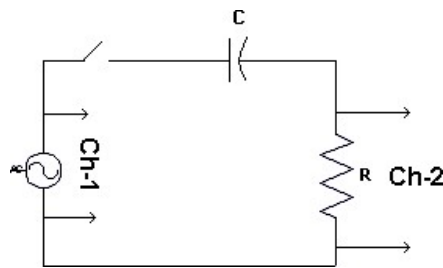


Figure-1

#### **Analysis of a Series RC Circuit**

For doing a complete analysis of a series RC circuit, given the values of R, C, f, and  $V_T$ .

Step 1: Calculate the value of  $X_C$ :

$$X_C = 1 / (2\pi fC)$$

Step 2: Calculate the total impedance  $Z$ :

$$Z = \sqrt{X_C^2 + R^2}$$

Step 3: Use Ohm's Law to calculate the total current  $I_T$ :

$$I_T = V_T / Z$$

### Difference between Rectangular & Polar representation of Impedance:

- In Rectangular form:

$$Z_T = R - j X_C$$

- In Polar form:

$$Z_T = \sqrt{R^2 + (X_C)^2}$$

$$\theta = \tan^{-1}(-X_C/R) = \tan^{-1}(-1/\omega RC)$$

### Impact of frequency on the value of capacitance:

Figure 2 will show the impact of frequency by varying the value of Capacitance in series resonance.

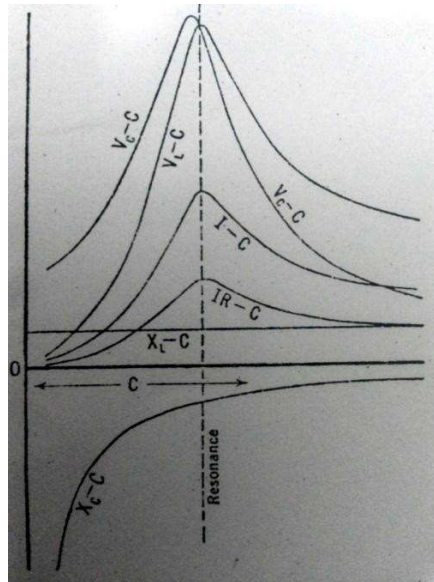


Figure-2

### RL Series Circuit:

A resistor-inductor circuit (RL circuit), or RL network, is an electric circuit composed of resistors and inductor in series driven by a voltage or current source (See the figure-3). A first order RL circuit is composed of one resistor and one inductor and is the simplest type of RL circuit.

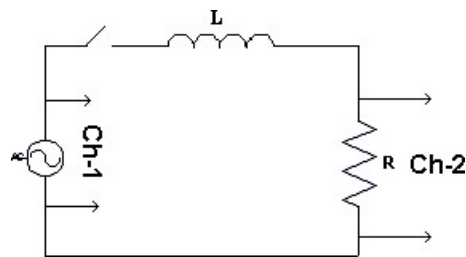


Figure-3

### Analysis of a Series RL Circuit

For doing a complete analysis of a series RL circuit, given the values of R, L, f, and  $V_T$ .

Step 1: Calculate the value of  $X_L$ :

$$X_L = 2\pi fL$$

Step 2: Calculate the total impedance Z:

$$Z = \sqrt{X_L^2 + R^2}$$

Step 3: Use Ohm's Law to calculate the total current  $I_T$ :

$$I_T = V_T / Z$$

### Difference between Rectangular & Polar representation of Impedance:

- In Rectangular form:

$$Z_T = R + j X_L$$

- In Polarform:

$$Z_T = \sqrt{R^2 + (X_L)^2}$$

$$\theta = \tan^{-1}(X_L/R) = \tan^{-1}(\omega L / R)$$

### Impact of frequency on the value of inductance:

Figure 4 will show the impact of frequency by varying the value of Inductance in series resonance.

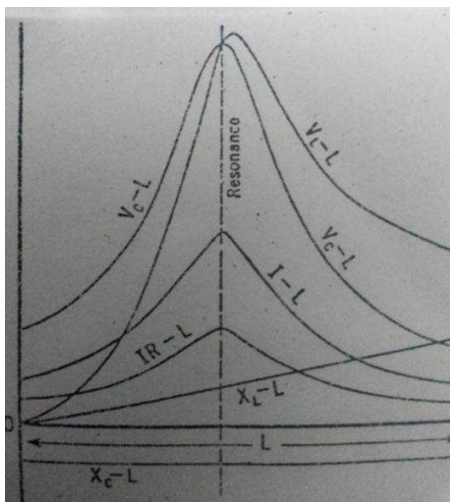


Figure-4

### **Pre-Lab Homework:**

Read about the characteristics of RC and RL series circuit from “Alternating Current Circuit” by George F Corcoran and use NI Multisim to generate the output of the circuits provided in this lab sheet. Compare the wave shapes given in the textbook with your results. Save the simulation results and bring it to the lab.

### **Apparatus:**

- Oscilloscope
- Function generator
- Resistor:  $100\Omega$
- Inductor:  $2.4\text{mH}$
- Capacitor:  $1\mu\text{F}/10\mu\text{F}$
- SPST switch
- Connecting wire.
- Bread board

### **Precautions:**

Connection of circuit should be done carefully, and oscilloscopes should be properly calibrated using the information provided at the calibration port before obtaining the wave shapes using the experimental set up.

### **Experimental Procedure:**

1. Construct the circuit as shown in the fig.1. Connect channel 1 of the oscilloscope across function generator and channel 2 of the oscilloscope across R.
2. Set the amplitude of the input signal 10V peak to peak and the frequency at 1 kHz. Select sinusoidal wave shape.



3. Measure peak value of both wave shapes.
4. Determine phase relationship between the waves.
5. Write down the wave equations for I and E.
6. Calculate resistance and reactance from the relevant data.
7. Do the same experiment setting input frequency 5kHz and 10kHz.
8. Complete the following table.

Table 1

f	E	I	$Z = \frac{E}{I}$ (Polar form)	Z (Rectangular form)	R	$X_L$	$V_R = IR$	$V_L = IX_L$
1KHz								
5KHz								
10KHz								

9. Now construct the circuit as shown in fig.3. Connect channel 1 of the oscilloscope across function generator and channel 2 of the oscilloscope across R.
10. Do the same procedure stated in 2 to 7. Complete the following table.

Table 2

f	E	I	$Z = \frac{E}{I}$ (Polar form)	Z (Rectangular form)	R	$X_C$	$V_R = IR$	$V_C = IX_C$
1KHz								
5KHz								
10KHz								

### **Simulation and Measurement:**

Compare the simulation results with your experimental data/ wave shapes and comment on the differences (if any).

### **Questions for report writing:**

1. Complete Table 1 and Table 2.
2. Calculate the value of  $X_C$ ,  $X_L$ , Z, I.
3. Draw the complete vector diagram for the RL and RC circuit.
4. Comment on the role of frequency to inductive reactance and capacitive reactance.

### **Discussion and Conclusion:**

Interpret the data/findings and determine the extent to which the experiment was successful in complying with the goal that was initially set. Discuss any mistake you might have made while conducting the investigation and describe ways the study could have been improved.



### **References:**

- [1] “Fundamental of Electric Circuit” by Aleksandre Sadiku
- [2] “Alternating Current Circuit” by George F Corcoran
- [3] <http://physics.bu.edu/~duffy/py106/ACcircuits.html>

## Experiment No. 2

**Title:** To determine an unknown Low Resistance using CROMPTON Potentiometer

### OBJECTIVE:

To measure low resistance by Crompton Potentiometer.


### APPARATUS:

Crompton potentiometer New Tech Type NTI – 501, two battery eliminators, two rheostats, two one way keys, one two way key, One Galvanometer, one known resistance of comparatively higher value and given small resistance.

### THEORY:

Let  $I$  current is passing through known resistance  $R$  of comparatively higher value  $R$  and small unknown resistance  $r$ . The balancing length corresponding to potential drop on  $R$  is  $l_1$ .

$$\therefore IR = \sigma l_1 \dots\dots\dots (1)$$

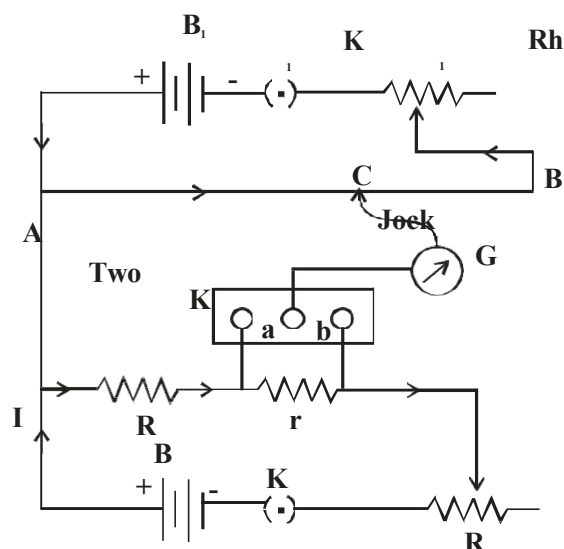

**Fig. 1**

Where  $\sigma$  is potential gradient.

If balancing length corresponding to potential drop on  $(R+r)$  resistance is  $l_2$ . Then I

$$(R + r) = \sigma l_2 \quad (2)$$

$$\begin{aligned} & \frac{(2)}{(1)} \\ & \frac{R + r}{R} = \frac{l_2}{l_1} \\ \text{or } 1 + \frac{r}{R} &= \frac{l_2}{l_1} \\ \text{or } \frac{r}{R} &= \frac{l_2 - l_1}{l_1} \\ \text{or } r &= \frac{l_2 - l_1}{l_1} R \dots\dots\dots (3) \end{aligned}$$

### **OBSERVATIONS:**

Sr. No.	Balancing length $l_1$ for P.D. on R Cm	Balancing length $l_2$ for P.D. on R Cm	$r$ (Ohm) <hr/>
1.			
2.			
3.			
4.			
5.			

### **CALCULATIONS:**


Putting values of  $l_1$ ,  $l_2$  and  $R$  in the formula the value of unknown small resistance  $r$  is calculated in each set of observations. Then mean value of  $r$  is determined.

### **RESULT:**

The value of given small resistance as determined using Crompton potentiometer is  
= ..... Ohm.


### **PRECAUTIONS:**

1. The E.M.F. of the cell used in primary circuit should be kept more than E.M.F. of the cell in secondary circuit.
2. All the positive terminals should be connected to the same point (A) of the potentiometer.
3. Jokey should not be moved along the potentiometer wire.
4. Electrical connections should be tight.

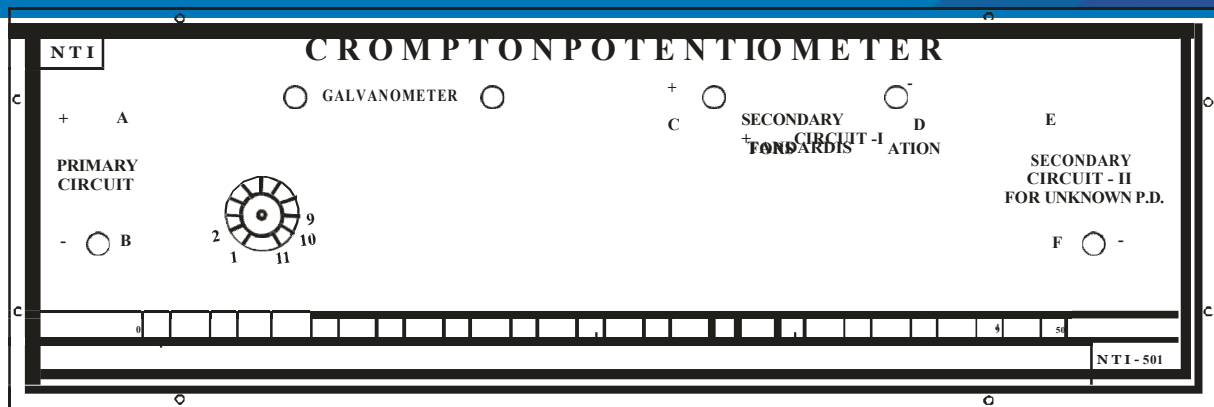

**Fig. (2) Panel Diagram**

\*\*\*\*\*

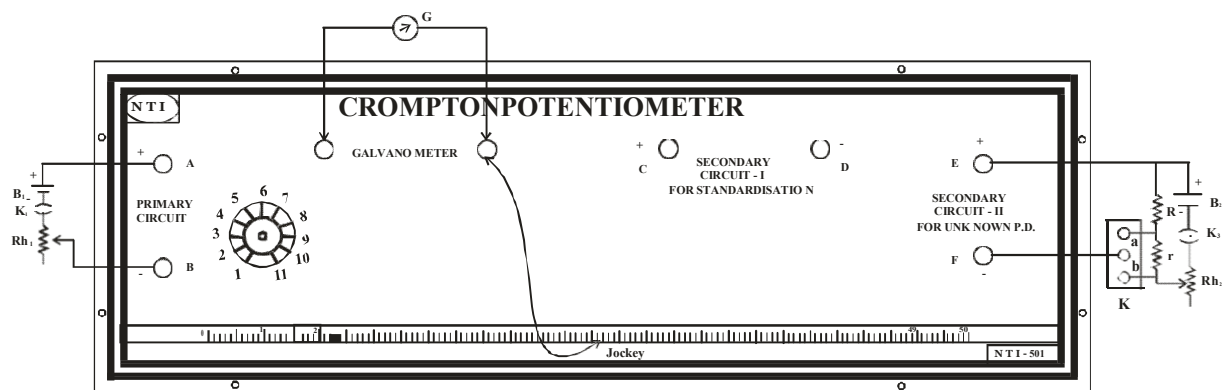

**Fig. (3) Connections for Crompton Potentiometer**

\*\*\*\*\*


### Experiment No. 3

**Aim: To find low resistance by Carey Fosters bridge**

**1. Apparatus required:** Given low resistance, dc power supply (2 V), Carey Foster's bridge, galvanometer, one waykey.

**2. Formula used:**  $X = \frac{d_2 Y_1 - d_1 Y_2}{d_2 - d_1}$

**3. Circuit Diagram:**

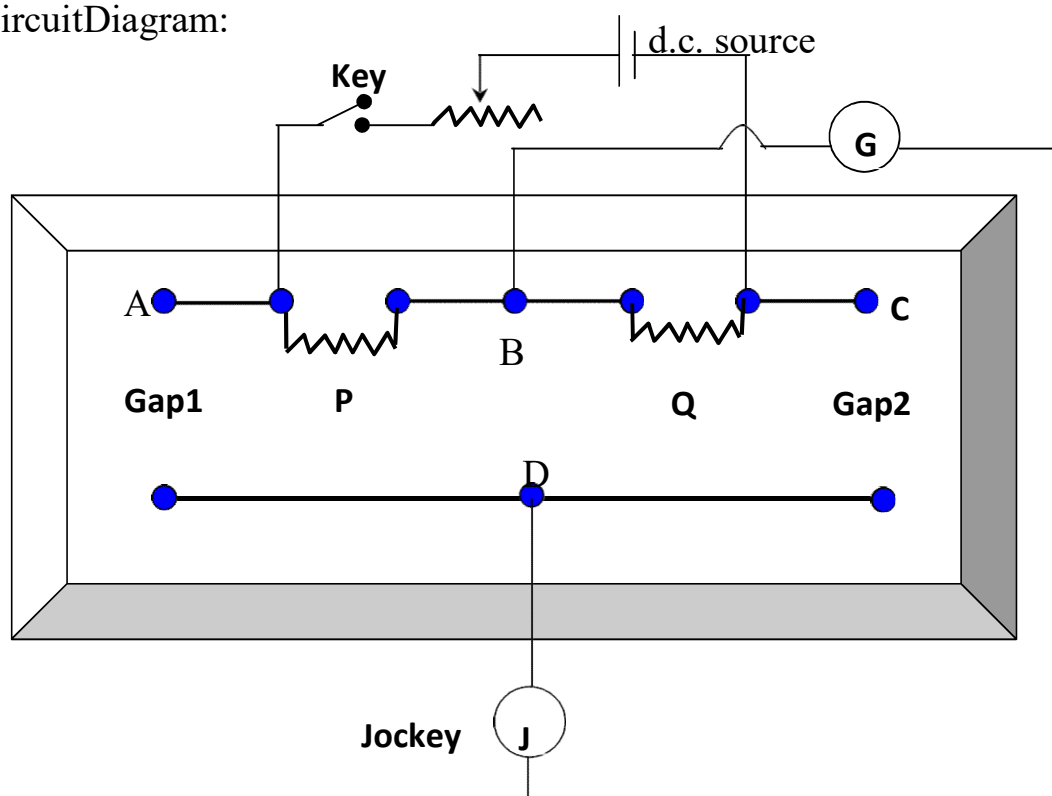

**4. Theory:** Carey Foster's bridge is a modified Wheatstone bridge. Here a potentiometer wire MN is inserted between the R and S arms of the Wheatstone bridge as shown in Fig. below. The ratio arms P & Q are made equal. Gap 1 carries a small resistance (known) and the Gap 2 (fourth arm) carries the unknown resistance. If  $\rho$  be the resistance per unit length of wire,  $r_1$  &  $r_2$  be the end resistances at M & N, MD =  $l_1$  is balancing length as shown in Fig.,

then,  $\frac{P}{Q} = \frac{X + l_1 \rho + r_1}{Y + (100 - l_1) \rho + r_2}$  .. (1) When, X & Y are interchanged, the balance point shifts to a

length  $l_2$ , then,  $\frac{P}{Q} = \frac{Y + l_2 \rho + r_1}{X + (100 - l_2) \rho + r_2}$  ..... (2)

Comparing (1) & (2) and adding 1 to both sides, we get,

$$\frac{X + Y + 100\rho + r_1 + r_2}{Y + (100 - l_1)\rho + r_2} = \frac{X + Y + 100\rho + r_1 + r_2}{X + (100 - l_2)\rho + r_2}$$

$$\Rightarrow X + (100 - l_2)\rho + r_2 = Y + (100 - l_1)\rho + r_2 \Rightarrow Y - X = (l_1 - l_2)\rho$$



Where X is unknown resistance,  $(l_1 - l_2)$  is shift in balance point when the positions of X & Y are interchanged. Let  $d_1$  &  $d_2$  are the shifts corresponding to resistances  $Y_1$  &  $Y_2$ , then,

$$X - Y_1 = d_1 \rho, \text{ and, } X - Y_2 = d_2 \rho, \text{ so, } \frac{X - Y_1}{X - Y_2} = \frac{d_1}{d_2} \Rightarrow X = \frac{d_2 Y_1 - d_1 Y_2}{d_2 - d_1}$$

## 5. Procedure:

- Make connection as shown in Fig.
- Fix  $P = Q = 1 \Omega$  throughout the experiment.
- Keep  $X = Y = 0$  by short circuiting by copper plates to get balance point.
- Repeat step (iii) by interchanging the position of copper plates and determine  $x_0$ .
- Replace trip of gap 1 by unknown resistance X and gap 2 by known resistance Y. Find balance point for  $0.1 \Omega$ , and, then interchange X & Y, and again find balance point.
- Repeat this step for  $Y = 0.2, 0.3, 0.4, 0.5 \Omega$ .

## 6. Observations: Determination of electrical zero:

Sr. No.	Resistance introduced in between		Position of Null point (cm)	Value of electrical zero, $x_0$ (cm) ( $x_0 = a - b$ )
	Gap-1	Gap-2		
1	Copper plate	Copper plate (a)		
2	Cu plates interchanged (b)			

## (b). Determination of unknown resistance:

Sr. No.	Y ( $\Omega$ )	Position of balance point with unknown resistance in		Shift $l_1 - l_2$ (cm)	Corrected shift $d = (l_1 - l_2) - x_0$ (cm)	Unknown resistance $X = \frac{d_2 Y_1 - d_1 Y_2}{d_2 - d_1}$ ( $\Omega$ )	Mean X ( $\Omega$ )
		Left gap $l_1$ (cm)	Right gap $l_2$ (cm)				
1							
2							
3							
4							
5							
6							

**7. Results:** The value of unknown resistance is .....  $\Omega$ .

## **8. Precautions:**

- (i). All terminals should be tight.

- (ii). The connecting wires and the copper strip should be thoroughly cleaned with sandpaper.
- (iii). The connection should be tight, and the plugs of the resistance box should be given twist so that they are tight.
- (iv). The battery key should be taken out when the readings is not being taken in order to avoid heating and the wire.

## Experiment No. 4


**Aim: To determine the resistance of Weston type galvanometer by Kelvin's method using Post Office box.**

**1. Apparatus required:** Post Office box, galvanometer, power supply (2v), Resistance box, connectingwires.

**2. Theory:** A post office box is a compact form of the Wheatstone's bridge. In the instrument each of the arms AB & BC contains three of 10, 100 and 1000  $\Omega$  respectively as shown in Fig.1. These are called ratio arms. The arm AD is the other ratio arm R. The key K1 is connected to the point A and the key K2 to the point B internally as shown by the lines drawn on the ebonite plate. The unknown, S, is connected between C & D, the battery, E, between C & A through the key K1 and the galvanometer, G, between D & B through the key K2. The circuit is now the same as shown in Fig.2. Hence,

$$\frac{P}{Q} = \frac{R}{G} \Rightarrow G = R \cdot \frac{Q}{P}$$

In the Kelvin's method the same galvanometer whose has to be measured, is also used as an indicator for obtaining the balance point. The galvanometer acts as its own indicator for obtaining the balance point as shown in Fig.3.

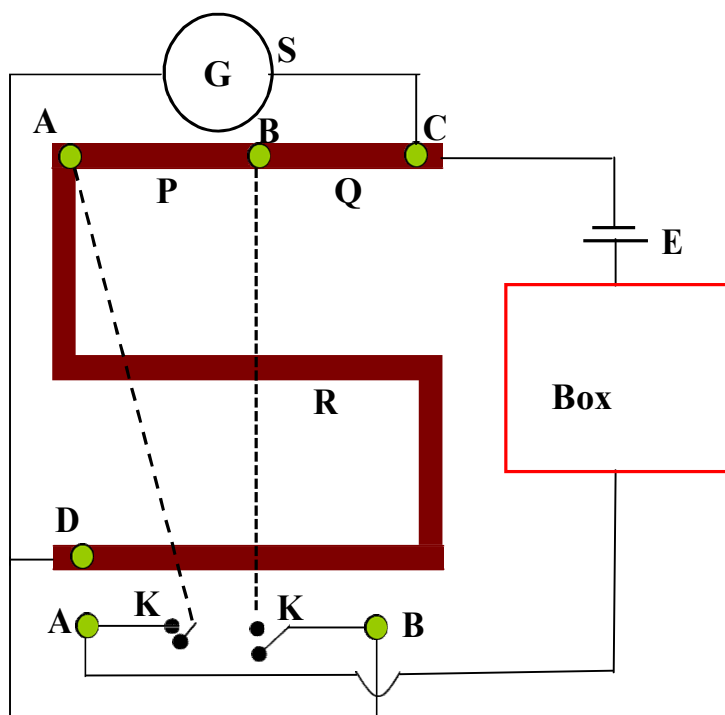

**Fig.1**

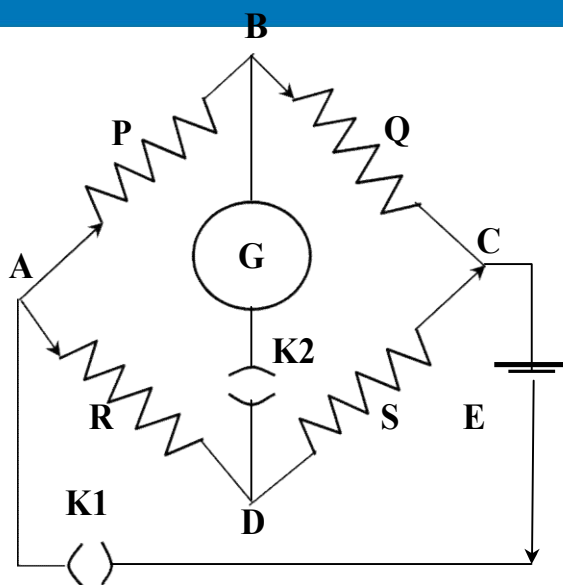


Fig.2

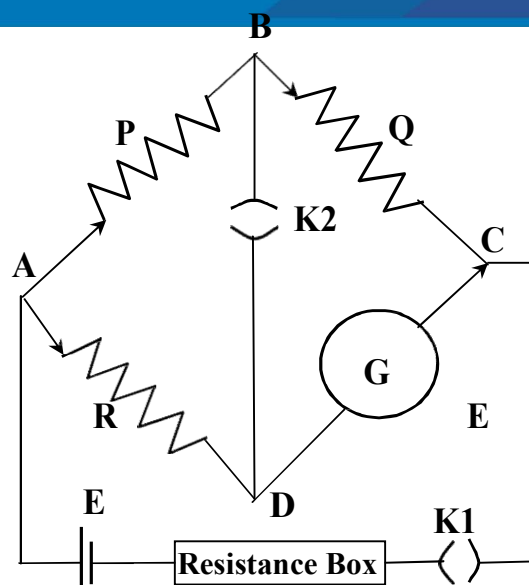


Fig.3.

### 3. Procedure:

- (i). Make connections as in Fig.1.
- (ii). Take resistance from box and keep other plugstight.
- (iii). Keeping  $R = 0$ , insert  $10\ \Omega$  s in arms P & Q. Press tappingkey K1 and adjust from resistance box so that deflection is between 10 &30.
- (iv). Insert  $10\ \Omega$  in R, press tapping K1 and note deflection in galvanometer. If deflection decreases on tapping key K2, go on repeating the observation byincreasing R in steps so that on pressing K1 first and then tapping K2, the deflection increases. The value of galvanometer lies between last two valuesof R.
- (v). Keeping  $Q = 10\ \Omega$  make  $P = 100\ \Omega$ . Starts with 10 times the lower value of R obtained in earlier step and increase it in steps, so that on pressing K1 first and then K2, the deflection increases instead of decreasing. Note last two values ofR.
- (vi). Keeping  $Q = 10\ \Omega$  make  $P = 1000\ \Omega$ . Starts with 10 times the lower value of R obtained in earlier step and increase it in steps, so that on pressing K1 first and then K2, the deflection increases instead of decreasing. Note last two values ofR.

#### 4. Observations:

Sr. No.	Ratio arms		Values of R ( $\Omega$ ) for which deflection increases instead of decreasing	G ( $\Omega$ ) lies between $G \equiv R \cdot \frac{Q}{P}$
	P ( $\Omega$ )	Q ( $\Omega$ )		

**5. Result:**TheresistanceoftheGalvanometeris ..... $\Omega$ .

#### 6. Precautions:

- (i). The ends of the connecting wires should be clean.
- (ii). All the plugs should be properly tight.
- (iii). K1 should be pressed first and thereafter K2.

## Experiment No. 5

### VERIFICATION OF THEVENIN'S AND NORTON'S THEOREMS

**AIM:** To Verify Thevenin's Norton's and Maximum power transfer theorems.




**APPARATUS:**

S.No	Equipment	Range	Type	Quantity
1.	Ammeter	0-200mA	MC	
2.	Voltmeter	0-20V	MC	
3.	Bread Board	-	-	1
4.	R.P.S	0-30V/0-1A	Dual channel	1
5.	Resistors			As required
6.	Connecting Wires			As required

### THEVENIN'S THEOREM

**STATEMENT:** - Any two terminal, linear, bilateral network having a number of voltage, current sources and resistances can be replaced by a simple equivalent circuit consisting of a single voltage source in series with a resistance, where the value of the voltage source is equal to the open circuit voltage across the two terminals of the network, and the resistance is the equivalent resistance measured between the terminals with all energy sources replaced by their internal resistances.

### CIRCUIT DIAGRAM:

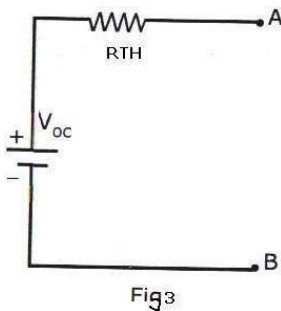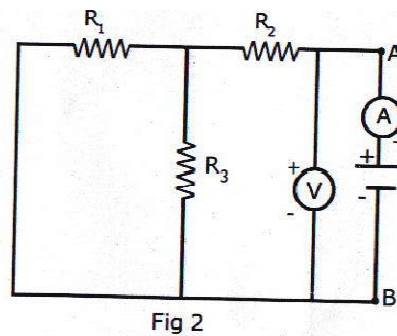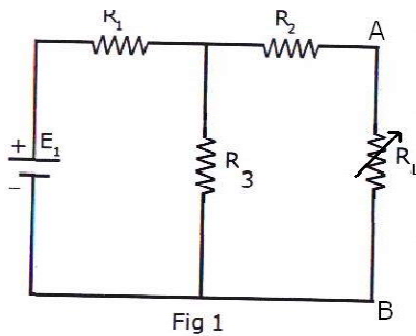

### PROCEDURE:


1. Connect the circuit diagram as shown in fig 1.
2. Measure  $V_{oc}$  between A and B terminals, by open circuiting AB terminals.
3. Connect the circuit as shown in fig 2.
4. The resistance between A and B is obtained by using voltmeter, ammeter method, and the ratio of V & I gives  $R_{Th}$
5. Draw the Thevenin's equivalent circuit as shown in fig 3



## NORTON'S THEOREM

**STATEMENT:** Any two terminals, linear, bilateral network with current sources, voltagesources and resistances can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance. The value of the current source is the short circuit current between the two terminals of the network and the resistance is the equivalent resistance measured between the terminals of the network with all the energy sources replaced by their internalresistances.

### Circuit Diagram:

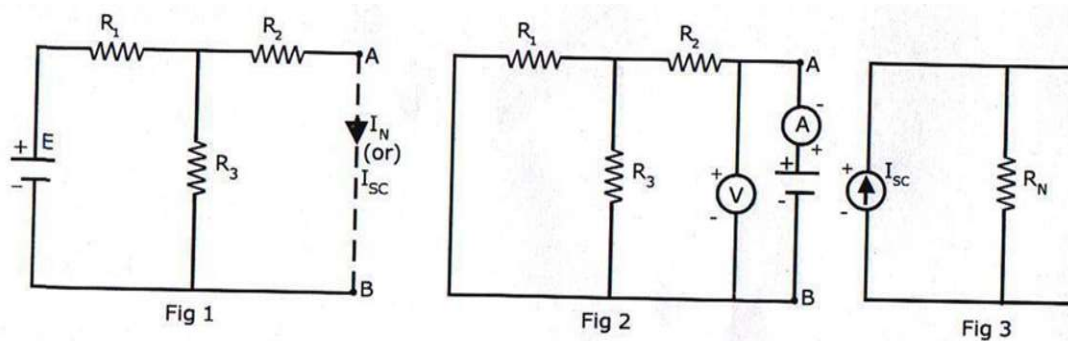

### PROCEDURE:

1. Connect the circuit diagram as shown in fig1.
2. Measure the current  $I_{sc}$  (or)  $I_N$  through 'AB' by short-circuiting the resistance between A and B.
3. Connect the circuit diagram as shown in fig2.
4. The resistance between A and B is obtained by using voltmeter, ammeter method and the ratio of  $V$  &  $I$  gives  $R_N$ .
5. Draw Norton's equivalent circuit by connecting  $I_N$  &  $R_N$  in parallel as shown in fig3.

**TABULAR COLUMN:**

<b>Parameters</b>	<b>Theoretical Values</b>	<b>Practical Values</b>
Voc		
Isc		
$R_{TH}$		

## Experiment No. 6

### SUPERPOSITION THEOREM AND RECIPROCITY THEOREM


#### AIM:


To Verify Superposition Theorem and to find the RMS value of complex wave form

#### APPARATUS:


S.No.	Equipment	Range	Type	Quantity
1.	Resistors	-	-	As required
2.	Multi-meter			1
3.	R.P.S	0-30V/0-1A	Dual channel	1
4.	Bread Board	-	-	1
5.	Connecting Wires			As required

#### CIRCUIT DIAGRAM:

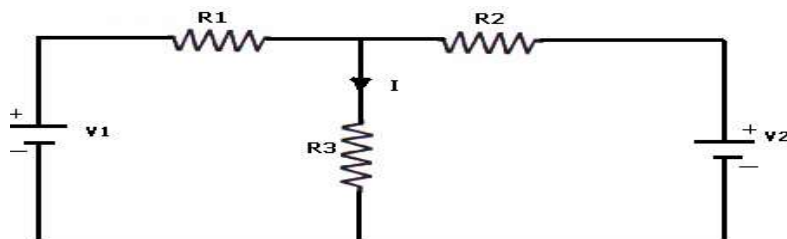

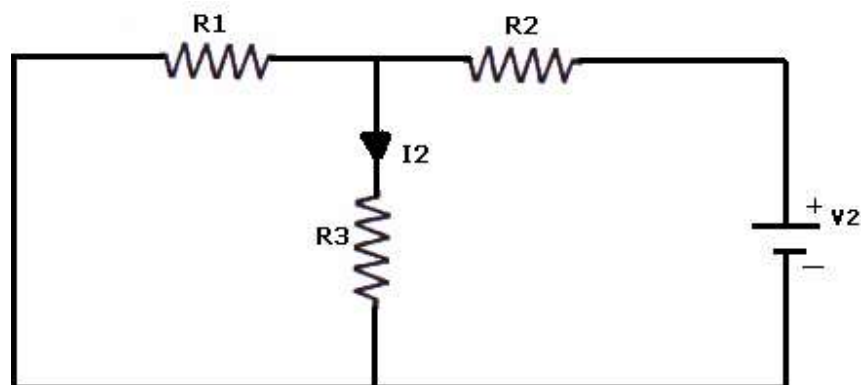

**Fig3**

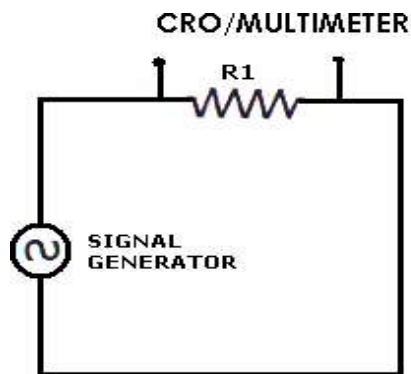

**Fig4**

### **PROCEDURE:**

1. Connect the circuit as shown in figure (1) and note down the current flowing through  $R_3$ , and let it be  $I$ .
2. Connect the circuit as shown in figure (2) and note down the ammeter Reading, and let it be  $I_1$ .
3. Connect the circuit as shown in figure (3) and note down the ammeter reading, and let it be  $I_2$ .
4. Verify for  $I = I_1 + I_2$ .
5. Compare the practical & theoretical currents.

### **RESULT:**

## VERIFICATION OF RECIPROCITY THEOREM

### AIM:

To verify Reciprocity theorem both analytically and experimentally.


### APPARATUS REQUIRED:

S.No.	Equipment	Range	Type	Quantity
1.	Resistors	-	-	As required
2.	Multi-meter			1
3.	R.P.S	0-30V/0-1A	Dual channel	1
4.	Bread Board	-	-	1
5.	Ammeter	0-200mA	MC	1
6.	Connecting Wires			As required

### THEORY:

**STATEMENT:** “In a linear bi-lateral single source network ,the ratio of excitation to the response is constant when the position of excitation and response are interchanged”.


### CIRCUIT DIAGRAM:

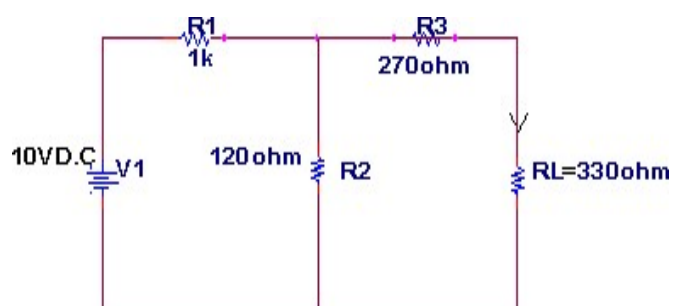

## CALCULATION:


Step i) Calculation of  $I_L$  before interchanging the power supply,

$$I_L = I_2 = 1.5\text{mA}$$

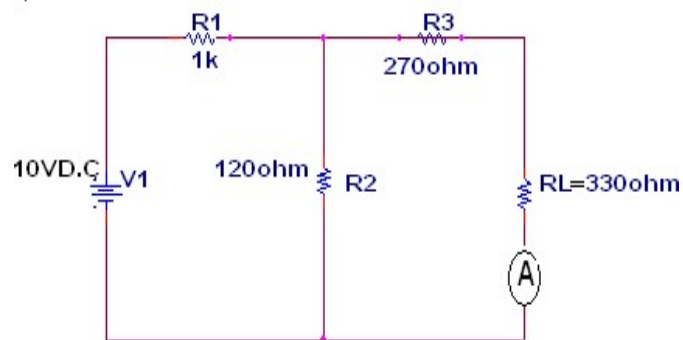

Step ii) Calculation of  $I_L$  after interchanging the power supply,  $I_L = I_2 =$

$$1.5\text{mA}$$

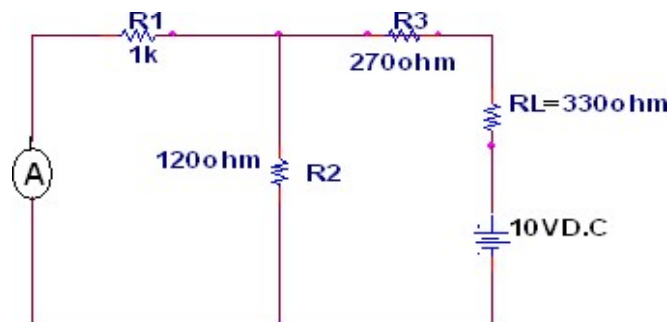

## PROCEDURE:

1. For the given circuit diagram, the theorem must be verified theoretically.
2. The ranges of the meters are selected according to the theoretical calculations.

3. Circuit connections are made as shown in figure.
4. Required supply is given to the circuit and the corresponding readings of ammeter and voltmeter are noted down.
5. Theoretical values are compared with practical values.

**TABULATION:**

Parameters	Analytically	Experimentally
$I_L$	1.5mA	
$I_{L,}$	1.5mA	
$V/I_L$	6.66K $\Omega$	
$V/I_{L,}$	6.66K $\Omega$	

**RESULT:**

## VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM

**AIM:** - To Verify Maximum power transfer theorem.


**APPARATUS:**

S.No.	Equipment	Range	Type	Quantity
1.	Resistors	-	-	As required
2.	Multi-meter			1
3.	R.P.S	0-30V/0-1A	Dual channel	1
4.	Bread Board	-	-	1
5.	Ammeter	0-200mA	MC	1
6.	Voltmeter	0-20V	MC	1
7.	Connecting Wires			As required

**STATEMENT:**

The maximum power transfer theorem states that maximum power is delivered from a source resistance to a load resistance when the load resistance is equal to source resistance.  $R_s = R_L$  is the condition required for maximum power transfer.

**Circuit Diagram:**

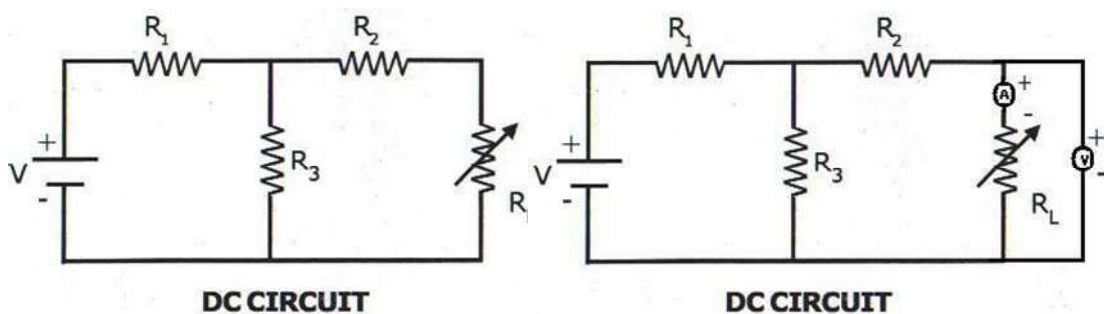




### PROCEDURE:

1. Connect the circuit as shown in fig.
2. Vary the load resistance in steps and note down voltage across the load and current flowing through the circuit.
3. Calculate power delivered to the load by using formula  $P=V \cdot I$ .
4. Draw the graph between resistance and power (resistance on X- axis and power on Y- axis).
5. Verify the maximum power is delivered to the load when  $R_L = R_s$  for DC.

### TABULAR COLUMN:

$R_L$	$V_L$	$I_L$	$P=VI$

### MODEL GRAPH:

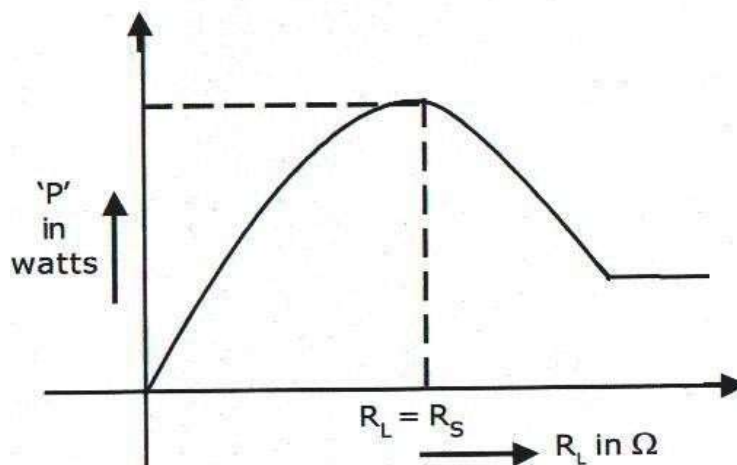

### RESULT:

## Experiment No. 7

# OPERATING INSTRUCTIONS FOR ANDERSON'S BRIDGE

### **OBJECT:**

To measure self-inductance of a coil using Anderson's Bridge.

### **APPARATUS:**

Anderson's Bridge has been designed on a training board New Tech Type NTI – 117. It consists three fixed resistances  $R_1$ ,  $R_2$ ,  $R_3$ .  $R_1$  is connected in between A and B.  $R_2$  is connected in between B and C. Thus  $R_1$  and  $R_2$  form two ratio arms,  $R_3$  is connected in between A and D and a variable resistance  $R_4$  is connected in unknown arm C and D. The inductance ( $L$ ) to be measured is also connected in the same arm. Thus,  $R_4$  and  $L$  are in series. A set of seven capacitors  $C = C_1, C_2, C_3, C_4, C_5, C_6, C_7$  and resistance  $r$  in two steps of (i)  $\times 100\Omega$  upto  $1K\Omega$  (ii)  $\times 1K\Omega$  upto  $10 K\Omega$  are provided on the board. Fixed frequency oscillator is connected in the bridge two terminal provided for this. A headphone or galvanometer fitted with diode is joined in between two terminals marked for this purpose. Three inductances  $L_1$ ,  $L_2$  and  $L_3$  are also provided on the board.  $L_1$  is between first and second terminal,  $L_2$  is between second and third terminal,  $L_3$  is in between third and fourth terminal.

### **THEORY:**

When Anderson Bridge is balanced in the sound in headphone or deflection in galvanometer fitted with diode is minimum. The potential at E & F is same then:

$$\therefore \frac{P}{Q} = \frac{R}{S}$$
$$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

And if  $P = Q$  or  $R_1 = R_2$

$$L = CR_3(R_2 + 2r) \dots\dots\dots (1)$$

**PROCEDURE:**

- (1) Connect oneself inductance say  $L_2$  (second and third terminals) to the sockets provided across the symbol of the Coil in the bridge circuit.
- (2) Connect a leclanche cell or lead accumulator in place of oscillator and Galvanometer at place of headphone. Adjust  $R_4$  so that Zero deflection is obtained in Galvanometer keeping  $r$  at 0 resistance.
- (3) Now disconnect leclanche cell and at its place connect fixed frequency oscillator. Headphone or Galvanometer fitted with diode is connected at its proper place.
- (4) Set suitable value of  $C$  and by changing  $r$  obtain minimum sound in headphone or minimum deflection in Galvanometer. Record the value of  $C$  and  $r$  in O.T.
- (5) Changing value of  $C$  repeat step (4) several times. Record the value of  $C$  and  $r$  in O.T.
- (6) Calculate  $L$  using formula (1) given in theory.

**OBSERVATIONS : Given Values :**

$$R_1 = R_2 = R_3 = 1K\Omega$$

$$C_1 = \dots\dots \mu F, C_2 = \dots\dots \mu F, C_3 = \dots\dots \mu F$$

$$C_4 = \dots\dots \mu F, C_5 = \dots\dots \mu F, C_6 = \dots\dots \mu F \text{ and } C_7 = \dots\dots \mu F$$

$$L_1 = \dots\dots mH, L_2 = \dots\dots mH, L_3 = \dots\dots mH$$

S. No.	Value of C $\mu F$	Resistance $r$ Ohms	Inductance $L$ mH
1			
2			
3			

Mean Value of L = ..... mH

**CALCULATIONS:**

$$\begin{aligned} L &= CR_3 (R_2 + 2r) \text{ Henry} \\ &= CR_3 (R_2 + 2r) \times 10^3 \text{ mH} \end{aligned}$$

**RESULT:**


Inductance of the given:

Coil = .... mH

Standard value = ....mH


**PRECAUTIONS:**

- (1) Initially the output of frequency oscillator should be kept low and near null point it should be increased.
- (2) If headphones are used there should be silence in the neighborhood.
- (3) For greater sensitivity of the bridge resistances in the four arms should be nearly same.
- (4) Plug type Resistance box or P.O. box should not be used.
- (5) For obtaining balance point  $L > CR_2R_3$ .
- (6) For inductance  $L_1$  is of low value  $C_1, C_2, C_3$  capacitors should be used. For inductance  $L_2$  is medium value  $C_3, C_4, C_5$ . Capacitors should be used and for  $L_3$  Capacitors  $C_5, C_6, C_7$  should be used to get null point and better results.

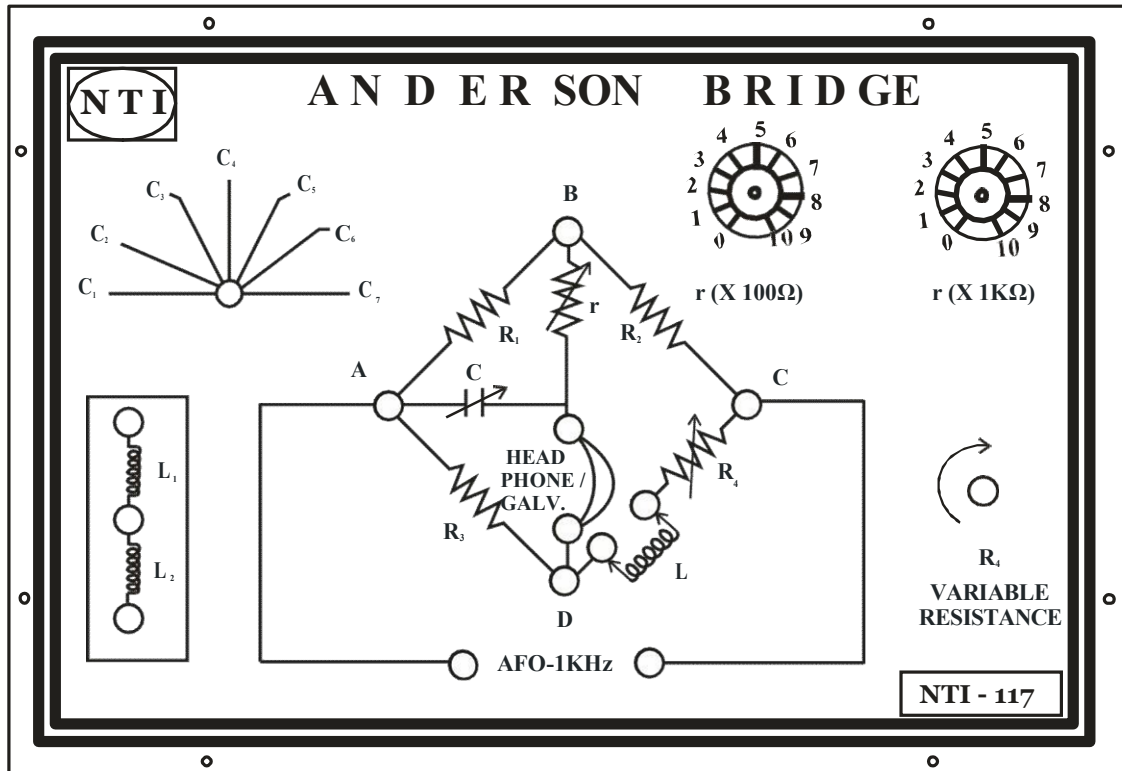

**Fig. (1) PanelDiagram**

\*\*\*\*\*

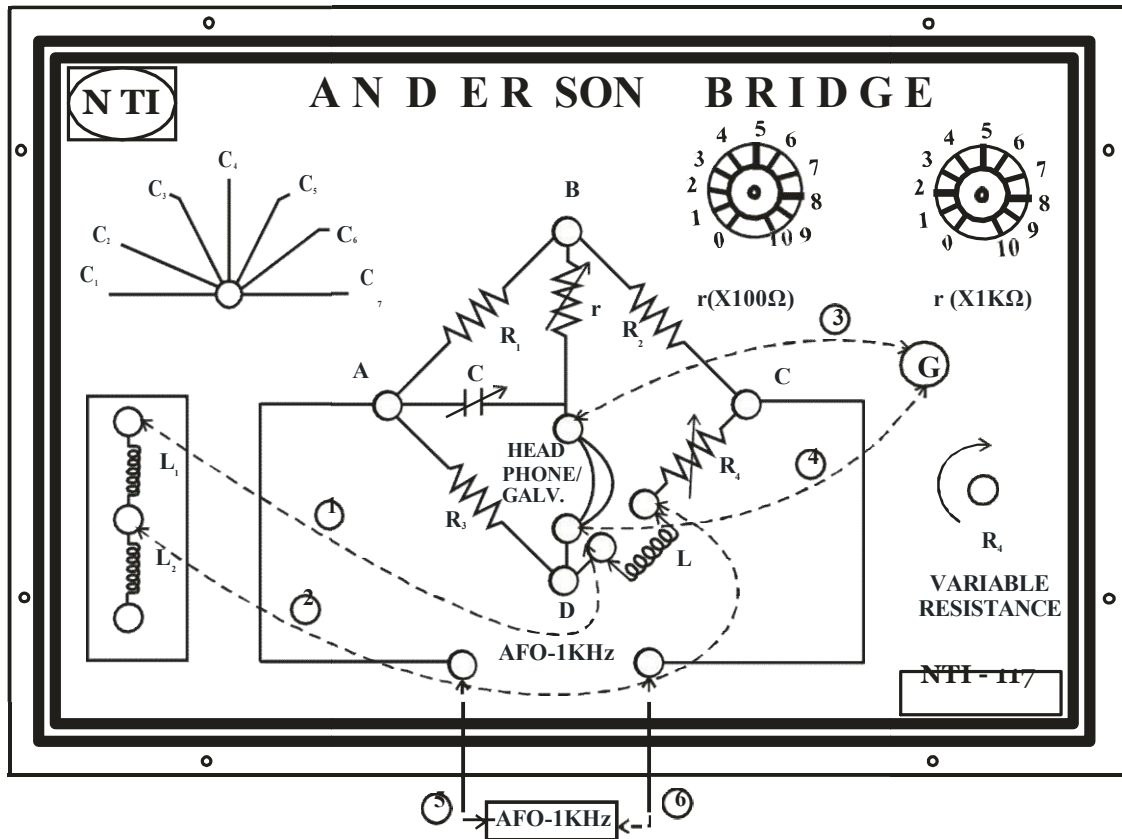

**Fig. (2) Connections for ANDERSON BRIDGE**

\*\*\*\*\*

## Experiment No. 8

### L-C-R Series and parallel

#### Resonance

**Aim**:- To study the frequency response and to find resonant frequencies of L-C-R series and parallel circuits. Also to find the quality factor and band width in L-C-R series circuit.

**Apparatus**:- A variable non-inductive resistor, a variable capacitor, a variable inductor, a signal generator, an a.c. milli-ammeter and the connecting wires.

**Formula** :- The resonance frequency  $f_0 = \frac{1}{2\pi\sqrt{LC}}$  Hz

Where L = Self inductance (mH)

C = Capacity of the capacitor (  $\mu$ F )

$$\text{Quality factor } Q = \frac{2\pi f_0 L}{R}$$

Where R = Resistance (  $\Omega$  )

Band width = (  $f_2 - f_1$  ) ( Hz )

$$\text{Also Quality factor } Q = \frac{f_0}{f_2 - f_1}$$

Where  $f_1$  and  $f_2$  are the frequencies at the half power points.

**Description and theory** :- (Series L-C-R) When the resistor R, inductor L and capacitor C are connected in series with a source of emf E, the circuit is called as the series resonant or series tuned circuit ( figure-1). This is an acceptor circuit, that means it allows maximum current to flow through it at a particular (resonant) frequency and at all other frequencies it allows less current.

In A.C. circuits the voltage and the current are usually out of phase. Across the inductor, the current lags behind the voltage by  $90^\circ$ , where as across the capacitor, the current leads the voltage by  $90^\circ$ . But across the resistor the voltage and current both are in

phase. Under certain conditions, the voltage and current are in phase, even though the circuit consists of L, C and R and the circuit behaves as a pure resistor. This phenomenon is called resonance. This occurs at a single frequency known as resonant frequency. At this frequency the capacitive reactance ( $X_C = 1/\omega C$ ) and the inductive reactance ( $X_L = \omega L$ ) are equal and opposite in direction. So they get cancelled each other and only resistance acts.

The impedance of the circuit is given by  $Z = R + j(\omega L - 1/\omega C)$

At resonance the reactive term disappears  $\omega L - 1/\omega C = 0$

The impedance is minimum i.e.  $Z = R$

The current is maximum  $I = E/R$

$$\text{So } \omega L = 1/\omega C$$

$$\omega_0 = \omega = 2\pi f_0 \quad 1$$

At this frequency the current is maximum and this frequency  $f_0$  is called resonant frequency. The circuit has selective properties. To compare selectivity or sharpness of resonance, a band of frequencies is chosen at which the current falls to  $\frac{1}{\sqrt{2}}$  times (half power points) of its maximum value. The frequency difference ( $f_2 - f_1$ ) between the half power points are called the bandwidth.

L-C-R parallel:- Parallel resonant circuit ( figure-2 ) is one in which one branch consists of an inductor L with associated resistor R and the other branch consists of a capacitor C. This is a rejector circuit, that means it rejects the current or allows minimum current to flow through it, at a particular (anti- resonant) frequency and it allows more current at



all other frequencies. So the circuit is not selective. But it is highly selective when energized from a high impedance generator.

The impedance of the circuit is given by

$$\frac{1}{Z} = \frac{1}{R+j\omega L} + \frac{1}{\frac{1}{j\omega C}}$$

At resonance the impedance is maximum.

The impedance at resonance

$$Z = \frac{L}{CR}$$

The anti-resonance frequency

$$f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} \frac{R^2}{L^2}} \text{ Hz}$$

If R-value is small, then

$$f_o = \frac{1}{2\pi \sqrt{LC}} \text{ Hz}$$

**Procedure** :- For L-C-R series, the circuit is connected as shown in the figure-1. The source resistance and the series resistance should be small. The output voltage of the signal generator is adjusted to be around 5V. The frequency of the signal generator is changed in steps and the corresponding current values are noted from the a.c. milliammeter. The readings are tabulated. The current values increase with the increase of frequency, up to the resonant frequency, further increase of frequency causes the decrease of current. The L, C and R values are noted to calculate the resonant frequency  $f_0$  and Q-factor, using the above formulae.

**Note** :- The experiment may be repeated with a different values of „R“. Here the  $f_0$  value is unchanged, but Q- factor value is changed.

**Graph**:- A graph is drawn for current against frequency. The frequency corresponding to maximum current is noted and it is the resonant frequency  $f_0$ . The frequencies  $f_1$  and  $f_2$  corresponding to half power points is noted and from it the bandwidth,  $(f_1 - f_2)$  is noted. From the values of  $f_0$ ,  $f_1$  and  $f_2$ , the quality factor,  $Q$  is calculated.

For L-C-R parallel, the circuit is connected as shown in the figure-2. The frequency of the signal generator is changed in steps and the corresponding current values are noted from the a.c. milli-ammeter. The readings are tabulated. But here, the current values decrease with the increase of frequency up to the anti-resonant frequency, further increase of frequency causes the increase of current. The anti-resonant frequency  $f_0$  is noted corresponding to the minimum current in the circuit.

**Graph**:- A graph is drawn for current against frequency. The frequency corresponding to minimum current is noted and it is the anti-resonant frequency  $f_0$ .

**Precautions**:- 1) The internal resistance of the source and series resistance should be small.

2) Before going to the experiment the resonant frequency should be calculated from  $L$  and  $C$  values so that to select the range of frequencies for observation.

**Results**:-

**Table-1**


L-C-R Series

S.No.	Frequency (Hz)	Current (mA)
1.		
2.		
3.		
20.		

**Table-2**

L-C-R Parallel

S.No.	Frequency ( Hz )	Current ( mA )
1.		
2.		
3.		
20.		

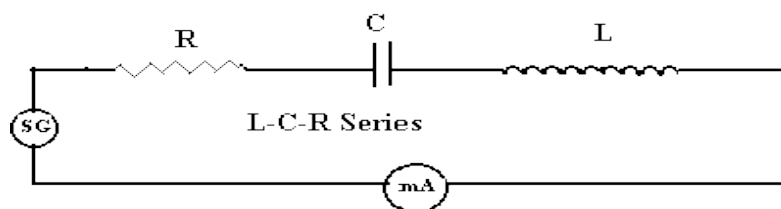**Fig-1****Fig-2**